

## Multiplexing the CS556x/7x/8x Delta-Sigma ADCs

### 1. INTRODUCTION

The CS556x/7x/8x devices represent a new generation of delta-sigma analog-to-digital converters that compete with SAR (successive approximation register) converters, with some distinct advantages. The unique features of these over-sampling converters allow them to be multiplexed at high speed across many input channels, because every conversion produces a fully settled result. In this application note the similarities and differences between SAR converters and the CS556x/7x/8x family of ADCs will be discussed as well as some design tips on choosing the right multiplexer and input amplifiers to drive these ADCs.

### 2. COMPARING THE CS556X/7X/8X WITH A SAR

Typically SAR ADCs have been used in the past for any high-throughput multiplexed application. This is because most delta-sigma converters require multiple conversions to fully settle. In other words, a large step change on the input takes a considerable amount of time to be reflected accurately (settled) in the output of the digital filter. Most delta-sigma converters use single-bit modulators and sample at kilohertz rates, and many samples are required as input to the digital filter to achieve the required accuracy. The CS556x/7x/8x family of converters is unique in that the modulator output is multi-bit and the sample rate is 8 MSps (megasamples per second). This, in combination with a specially designed FIR filter that only takes a few clock cycles to compute a result, produces a converter that can fully settle in a single conversion.

There are several distinct advantages of delta-sigma converters over SAR converters such as their superior DNL (differential non-linearity) performance and excellent noise immunity. One of the main reasons for the increased noise immunity is that the digital filter attenuates the out-of-band noise. However, a SAR ADC typically has a bandwidth much higher than Nyquist, and out-of-band noise can alias down into the pass band. Another reason is that a SAR converter samples the input signal once per conversion (Figure 1a) while the delta-sigma converter averages many samples per conversion (Figure 1b). As can be seen in Figure 1a, a noisy input signal (one with noise transients as illustrated) can result in significant errors within a SAR ADC unless multiple conversions are taken and averaged in software. In Figure 1b, the delta-sigma converter does this internally in the digital filter resulting in a conversion much less susceptible to transient noise.

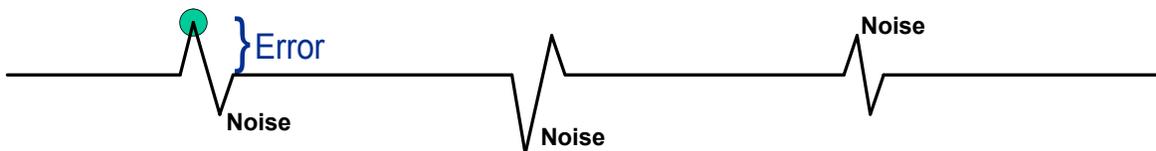


Figure 1a. SAR ADC Sampling (One Sample per Conversion)


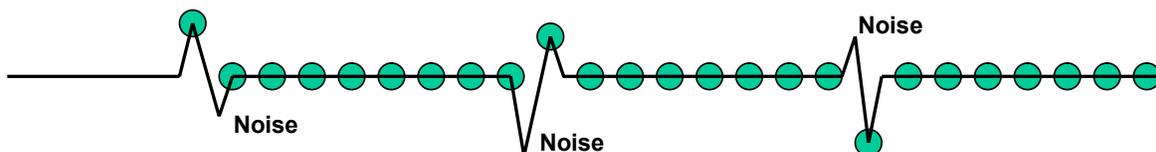


Figure 1b. Delta-Sigma ADC Sampling (Many Sample per Conversion)


### 3. REQUIREMENTS FOR MULTIPLEXING THE CS556X/7X/8X

For higher-throughput in multiplexed applications, it is desirable for the converter to fully settle on each conversion. In other words, the digital filter's output must accurately reflect the analog value on the input during the conversion. Additionally, the input multiplexer and any buffer amplifiers must be settled to the full accuracy of the converter before the samples are taken. This requires both the converter and the analog input circuitry to be fast settling. This is especially true if any amplifier or anti-aliasing resistor and capacitor is placed between the multiplexer and the ADC as illustrated in Figure 2. With a multiplexer it is possible for the ADC input to see a full-scale change from one conversion to the next. Any amplifier, or RC time constant due to resistance and capacitance, between the multiplexer and the ADC must fully settle to the new value before the sampling begins.

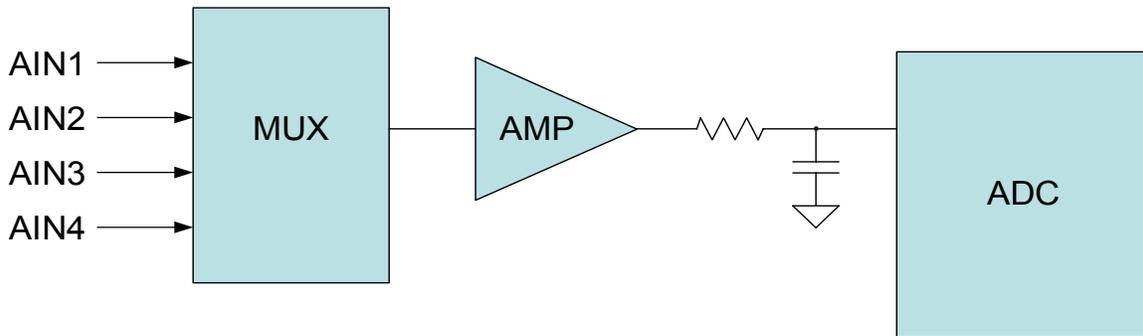


**Figure 2. Amplifier and Filter between Multiplexer and ADC**

With high-throughput converters like the 50 kSps CS5560/61, 100 kSps CS5570/71, or the 200 kSps CS5580/81 the circuit must settle in less than 10 MCLK periods (625 nanoseconds). The multiplexer before a SAR converter can be switched to the next channel after the conversion begins since the signal has already been sampled. However, many SAR ADC data sheets warn that a certain "quiet" period should be observed to prevent coupling of noise. The CS556x/7x/8x requires that the multiplexer be switched at the end of the conversion, since it is taking multiple samples of the input signal during the conversion (see Figure 3).

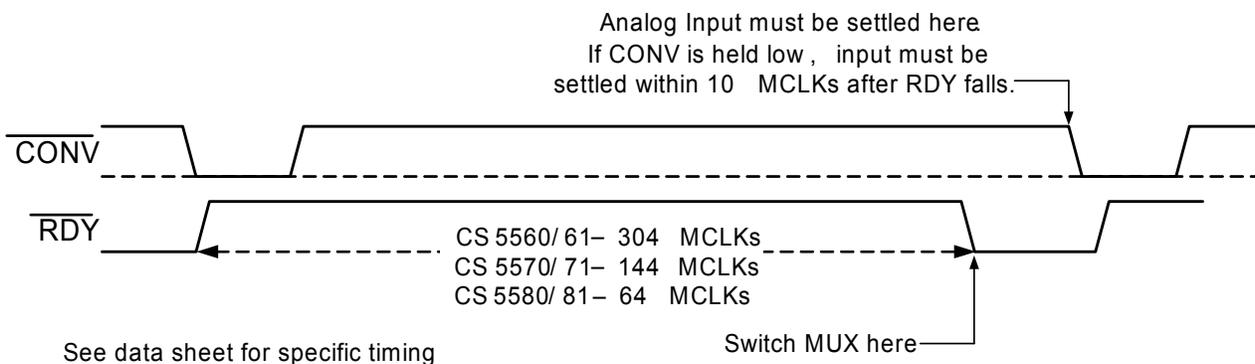

**Figure 3. Multiplexer Timing Requirements**

Therefore, an alternative should be considered where the amplifiers and anti-aliasing capacitors are on the input of the multiplexer. This generally requires a multiplexer with very low "on" resistance but the benefits are that the amplifier(s) and RC networks do not have to settle from possible large step changes when the multiplexer switches to another input. Figure 4 illustrates this arrangement.

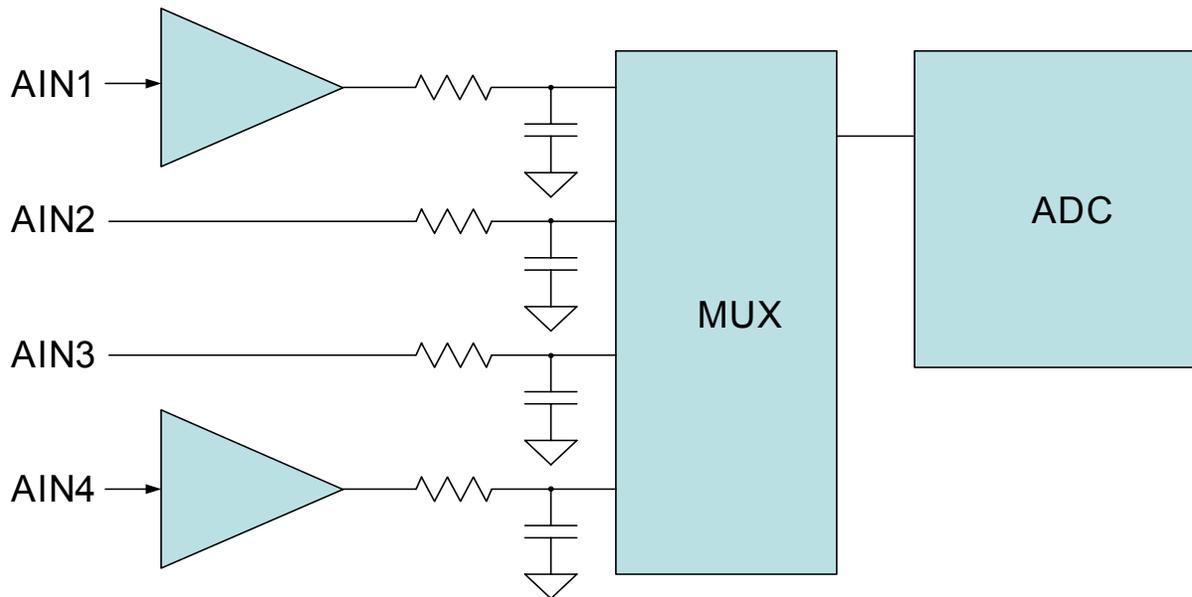

**Figure 4. Amplifier(s) and Filter(s) Placed Before Multiplexer**

As illustrated, not every input may require an amplifier or buffer. This is because there is an on-chip buffer in the CS556x/7x/8x. This rough charge buffer minimizes the sampling current on the input by charging the internal sample capacitor to a value very close to the input voltage using current from the supply pins rather than the input pin. This results in much higher effective impedance on the analog input. Where the full-scale range needs to be changed, an amplifier with gain or attenuation can be used.

## 4. SELECTING A MULTIPLEXER

There are several key parameters that need to be considered when selecting a MUX device. These include the “on” resistance, on/off capacitance, and switching speed. The on resistance should be as low as possible in order to assure that the input of the ADC fully settles on every sample. The inputs of modern converters consist of an analog switch and a sample capacitor. For most SAR converters this sample capacitor (or array of capacitors) is in the 70 pF to 100 pF range and must be charged once per conversion. For the CS556x/7x/8x, the input sample capacitor is only 4 pF but it is sampled once every 125 nanoseconds (8 MHz sample frequency). The CS556x/7x/8x also includes a rough-charge buffer which charges the sample capacitor to near its final value before switching the sample capacitor directly to the input pin for the fine-sample period. This greatly increases the effective input impedance of the device. However, this fine-sample period is only 20 nanoseconds out of each 125-nanosecond sample period, so excessive resistance in the input path may result in inadequate settling. Another reason the on resistance should be kept low is that the on resistance of a multiplexer is nonlinear across the full-scale range of the ADC and this may result in distortion. The lower the on resistance, the less distortion will result from this nonlinearity. As a general rule, an on resistance of less than 10 ohms should be used in order to minimize settling delays in charging the sample capacitance of the ADC.

The second parameter that should be considered is the channel capacitance or the on and off capacitance of the multiplexer. Typically the inputs or source of a multiplexer have a capacitance of 5 pF to 20 pF when the switch is open. However, when an input switch closes, additional capacitance is added from the other analog-switch channels that are part of the multiplexers output/drain. This capacitance typically increases as the number of multiplexer inputs increase. For example, a 16-to-1 MUX will usually have a higher drain capacitance than an 8-to-1 MUX. What needs to be considered here is that the output-channel capacitance will always be charged to the previously

selected input's voltage level and this charge will be dumped into the next input's source when that switch closes. If an op-amp or high-impedance source is used for the input to the MUX, there could be an issue with settling when this charge is transferred through the switch. One of the functions of the anti-alias capacitor on the input side of the MUX in Figure 3 is to provide a reservoir of charge to the switch-channel capacitance. This is another reason why the on resistance of the MUX should be as low as possible – so the channel capacitance can be charged quickly. However, there is an inverse relationship between on resistance and channel capacitance because low on resistance requires larger transistors and larger transistors result in higher channel capacitance. The following table shows some examples of MUX devices along with their critical parameters. The devices grayed out are not recommended due to the parameters indicated.

**Table 1: Critical Parameters of Typical Multiplexers**

Part Number	# of Poles	# of Inputs	On/Off Speed ns	On Res Ohms	Off Cap pF	On Cap pF	Supply Voltage
ADG706	1	16	50/14	2.5	13	200	1.8 to 5.5
ADG707	2	8	50/14	2.5	13	100	1.8 to 5.5
ADG787	2	2	22/6	2.5	16	40	1.8 to 5.5
ADG884	2	2	53/21	0.28	103	295	1.8 to 5.5
DG406	1	16	134/98	60	6	114	±5 to ±20
DG407	2	8	134/98	60	6	57	±5 to ±20
DG408	1	8	150/150	100	3	37	±5 to ±20
DG409	2	4	150/150	100	3	25	±5 to ±20
HI-506	1	16	250/250	180	10	62	±15
HI-507	2	8	250/250	180	10	40	±15
HI-508	1	8	250/250	180	10	27	±15
HI-509	2	4	250/250	180	10	22	±15
ISL43L220	2	2	12/5	0.23	115	224	1.1 to 4.5
MAX306	1	16	130/55	60	8	140	±4.5 to ±20
MAX307	2	8	130/55	60	8	70	±4.5 to ±20
MAX4617	1	8	7/4.5	8	5	32	2 to 5.5
MAX4618	2	4	7/4.5	8	5	21	2 to 5.5
MAX4635	2	2	12/5	2.5	9	32	1.8 to 5.5


**Notes:**

1. Devices in gray are not recommended for this application due to the indicated parameters.
2. Parameters are typical values and are for comparative purposes only.
3. The manufacturer's data sheet should be referenced for min and max values

The third parameter to be considered when selecting a MUX is the switching speed. What needs to be considered here is the total time from when the system selects another channel to when the conversion can begin. This includes MUX turn-on time and analog circuitry settling time. For example, if it is desired to convert with the CS556x at its maximum speed of 50 kSps (CONV held low), then from the time the RDY signal falls until the next conversion begins is 10 MCLKs (at 16 MHz) or 625 nanoseconds. This means that the MUX channel must change as RDY falls and its turn on time and all analog settling must occur in less than 625 nanoseconds. If a MUX requires 250 nanoseconds to turn on, there is only 375 nanoseconds for the analog circuitry to settle. If more settling time is required, the CONV pin timing can be delayed to slow down the conversion rate, allowing enough delay after the MUX channel is changed to ensure complete settling.

The type of multiplexer selected will depend upon whether the converter is a single-ended-input or a differential-input ADC. The advantage of using a differential ADC rather than one with a single-ended input is an improvement

of approximately 6 dB in the full-scale signal-to-noise ratio. This is because the full-scale input range of the differential input devices is twice that of the single ended devices. For example the CS5560/70/80 has a differential input range of 8.192 volts ( $\pm 4.096$ ) while the CS5561/71/81 has a full-scale input range of 4.096 volts ( $\pm 2.048$ ). For an equivalent internal noise, this means the full-scale input-to-noise ratio improves by 6 dB when using the differential input devices. Of course, in order to take advantage of the differential device, the signal being converted needs to be a true differential signal that utilizes the full-scale range. Otherwise, a single-ended-to-differential conversion circuit would need to be designed using a low-noise op-amp such as illustrated in [Figure 5](#).

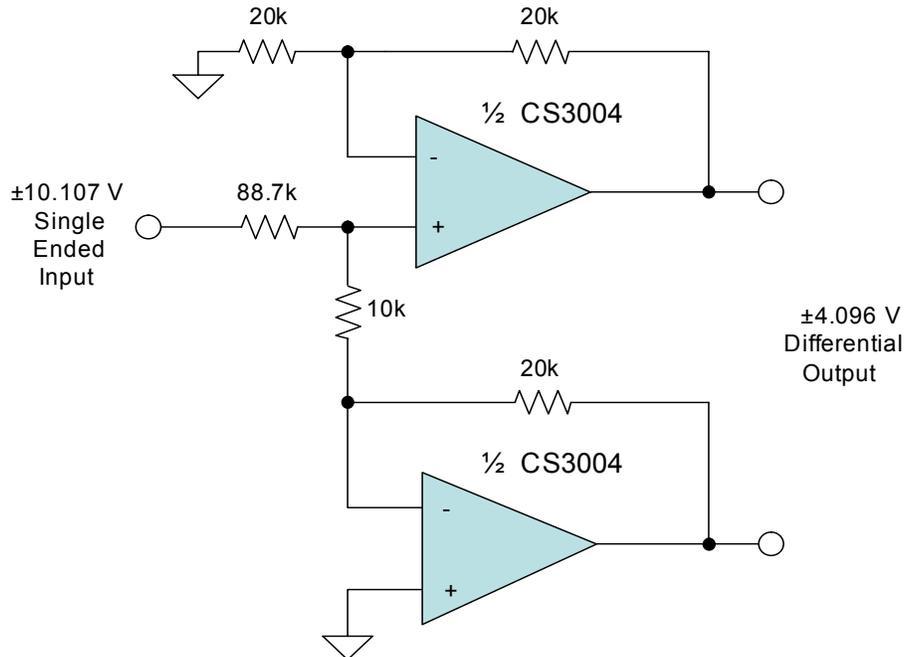

**Figure 5. Single-ended-to-differential Conversion Circuit**


If the decision is made to use a differential input ADC then the MUX will need to be a dual-pole device. Otherwise, for simpler implementations with less stringent noise performance requirements, a single-ended input device can be used with a single-pole MUX.

## 5. SELECTING AN AMPLIFIER

If an amplifier is needed to change the full-scale range or to buffer the inputs and it is placed between the MUX and the ADC, one of the most critical parameters will be settling time. However, as mentioned above, if the amplifier is placed before the MUX (one on each input of the MUX where needed) this requirement is greatly relaxed. In this case, signal-to-noise, distortion, DC offset, and stability over temperature become the primary selection criteria for most applications. Each application will determine which parameters are most critical so it becomes difficult to specify an op-amp and circuit configuration that will work in all situations. The CS3003 and CS3004 operational amplifiers will be suitable for many applications due to their excellent DC performance, moderate bandwidth, and low noise.


## 6. OPTIMIZED CIRCUITS FOR MULTIPLEXING CS556X/7X/8X ADCs

The following are examples of circuits that optimize the performance of the CS556x/7x/8x family of high-throughput ADCs for a number of general-purpose applications. Each circuit is followed by a brief circuit description with the key selection criteria noted.

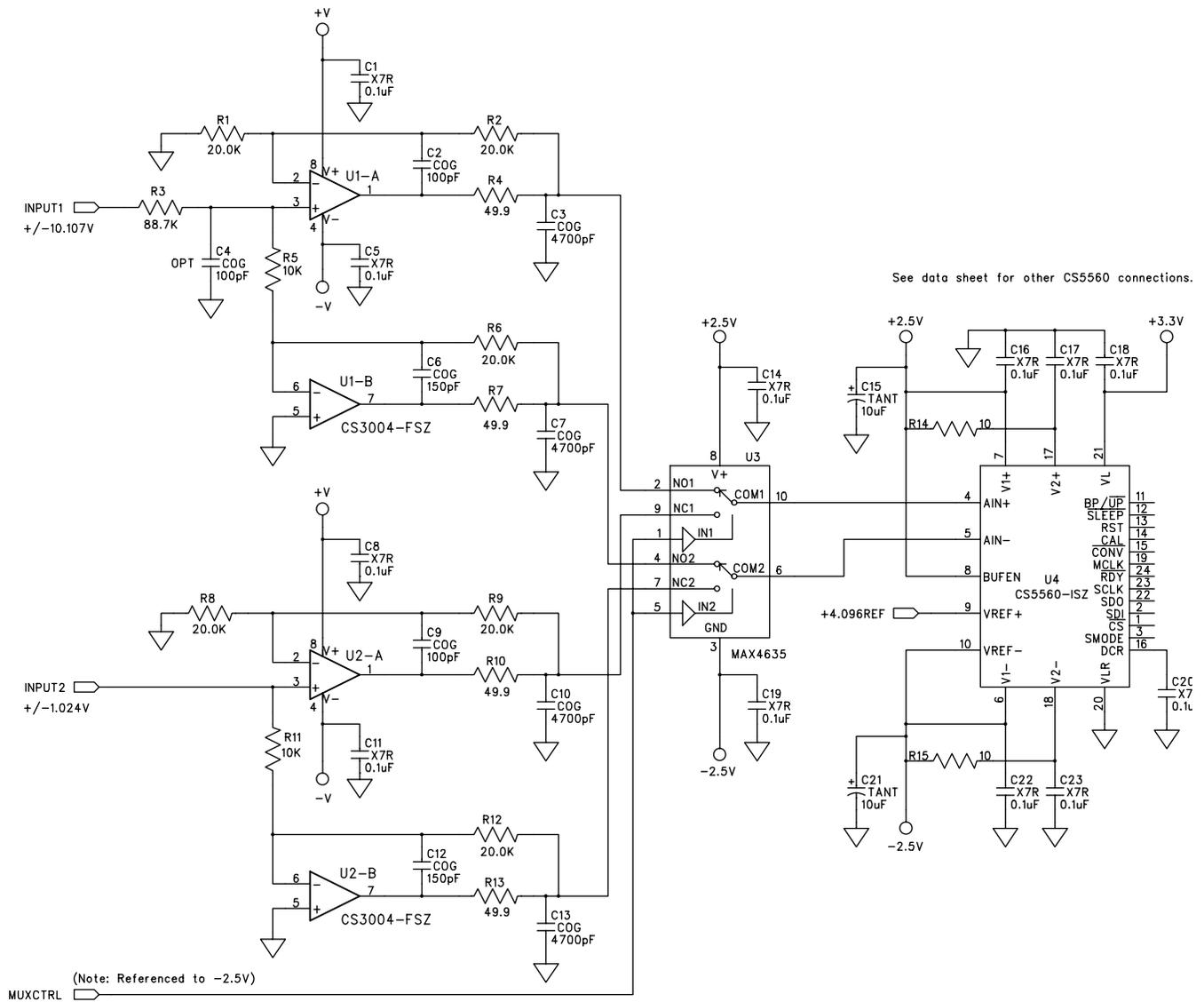

**Figure 6. 2-input, Single-ended-to-differential, Multiple Input Range, Multiplexed System**

In **Figure 6**, the differential device, CS5560, is multiplexed between two inputs which use single-ended-to-differential conversion circuits. As illustrated, each of these circuits can be configured to attenuate or amplify the single-ended input signal to use the full-scale range of the converter which is differentially  $\pm 4.096V$ . C4 is an optional capacitor which can be used to attenuate out-of-band noise to improve overall noise performance. The corner frequency with the components shown is 18 kHz. The 100 pF to 150 pF capacitors in the feedback of each amplifier are required to compensate for the capacitive load of the 4700 pF capacitors on the inputs of the multiplexer. The 4700 pF capacitors provide a charge reservoir for the switched-channel capacitance of the multiplexer and also provide dynamic input current when the converter samples.

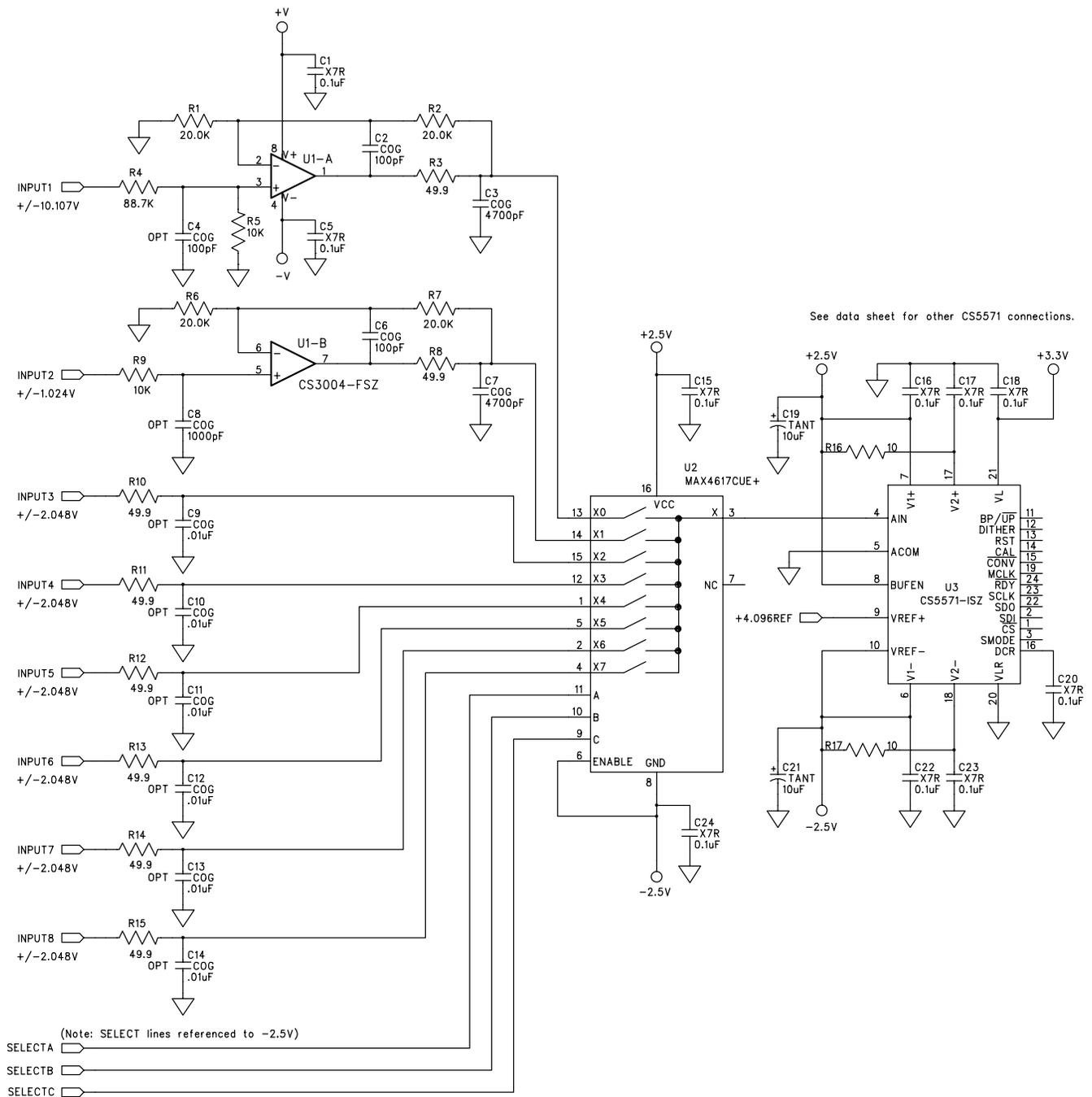

**Figure 7. 8-input, Single-ended, Multiple Input Range, Multiplexed System**

The circuit shown in [Figure 7](#) is similar to the differential circuit except there is no need to convert the single-ended input signal to differential. As mentioned previously, there will be a loss of approximately 6 dB in noise performance using the single-ended input device, since the full-scale input is half that of the differential device. As illustrated, not every input may need a buffer and if the source impedance is very low, better performance may be obtained without a buffer. In order to maintain DC accuracy, the series resistance in the unbuffered inputs needs to be kept very low. The key in this configuration is to keep the impedance between the ACOM pin of the ADC and the source signal as low as possible. Any current flowing in this return path will result in errors since there is no common-mode rejection with a single-ended device.

## **7. CONCLUSION**

The CS556x/7x/8x family of devices offers an exceptional alternative to SAR devices in multiplexed applications. Due to their digital filter with single-conversion settling, the input to the ADC can change from one end of full scale to the other between conversions and still maintain full accuracy. Since delta-sigma converters have far superior differential non-linearity (DNL) specifications and excellent noise performance, they provide a performance upgrade path from conventional SAR ADCs. They also offer 24-bit resolution which is unattainable with SAR devices today.

---

## REVISION HISTORY

Release	Date	Changes
REV1	AUG 2007	Initial Release

---

### Contacting Cirrus Logic Support

For all product questions and inquiries, contact a Cirrus Logic Sales Representative.

To find the one nearest to you, go to <http://www.cirrus.com>

---

#### IMPORTANT NOTICE

Cirrus Logic, Inc. and its subsidiaries ("Cirrus") believe that the information contained in this document is accurate and reliable. However, the information is subject to change without notice and is provided "AS IS" without warranty of any kind (express or implied). Customers are advised to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, indemnification, and limitation of liability. No responsibility is assumed by Cirrus for the use of this information, including use of this information as the basis for manufacture or sale of any items, or for infringement of patents or other rights of third parties. This document is the property of Cirrus and by furnishing this information, Cirrus grants no license, express or implied under any patents, mask work rights, copyrights, trademarks, trade secrets or other intellectual property rights. Cirrus owns the copyrights associated with the information contained herein and gives consent for copies to be made of the information only for use within your organization with respect to Cirrus integrated circuits or other products of Cirrus. This consent does not extend to other copying such as copying for general distribution, advertising or promotional purposes, or for creating any work for resale.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). CIRRUS PRODUCTS ARE NOT DESIGNED, AUTHORIZED OR WARRANTED FOR USE IN AIRCRAFT SYSTEMS, MILITARY APPLICATIONS, PRODUCTS SURGICALLY IMPLANTED INTO THE BODY, AUTOMOTIVE SAFETY OR SECURITY DEVICES, LIFE SUPPORT PRODUCTS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF CIRRUS PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK AND CIRRUS DISCLAIMS AND MAKES NO WARRANTY, EXPRESS, STATUTORY OR IMPLIED, INCLUDING THE IMPLIED WARRANTIES OF MERCHANTABILITY AND FITNESS FOR PARTICULAR PURPOSE, WITH REGARD TO ANY CIRRUS PRODUCT THAT IS USED IN SUCH A MANNER. IF THE CUSTOMER OR CUSTOMER'S CUSTOMER USES OR PERMITS THE USE OF CIRRUS PRODUCTS IN CRITICAL APPLICATIONS, CUSTOMER AGREES, BY SUCH USE, TO FULLY INDEMNIFY CIRRUS, ITS OFFICERS, DIRECTORS, EMPLOYEES, DISTRIBUTORS AND OTHER AGENTS FROM ANY AND ALL LIABILITY, INCLUDING ATTORNEYS' FEES AND COSTS, THAT MAY RESULT FROM OR ARISE IN CONNECTION WITH THESE USES.

Cirrus Logic, Cirrus, and the Cirrus Logic logo designs are trademarks of Cirrus Logic, Inc. All other brand and product names in this document may be trademarks or service marks of their respective owners.