

High Performance Synchronous Buck EVM Using the TPS53124

Contents

1	Description.....	1
2	Electrical Performance	2
3	Schematic.....	3
4	Test Setup and Results	4
5	Configuration	5
6	EVM Assembly Drawing and PCB Layout.....	6
7	List of Materials	10
8	Reference	10

List of Figures

1	TPS53124 EVM Schematic Diagram	3
2	Equipment Setup for HPA332 EVM Board	4
3	1.05V Startup Waveforms	5
4	1.8V Startup Waveform	5
5	1.05V Load Transient Response	5
6	1.8V Load Transient Response	5
7	Top Assembly	6
8	Bottom Assembly	7
9	Top Layer	8
10	Inner Layer 1	8
11	Inner Layer 2	9
12	Bottom Layer	9

List of Tables

1	Electrical Performance	2
2	List of Materials	10

1 Description

The TPS53124 is a dual, adaptive on-time D-CAP™ mode synchronous buck controller. TPS53124 enables system designers to cost effectively complete the suite of DTV POL regulator and Digital STB regulator with a low external component count. The main control loop for the TPS53124 uses the D-CAP mode that is optimized for low ESR output capacitors such as POSCAP, SP-CAP, or High Polymer Chemistry and provides fast transient response with no external compensation. TPS53124 provides conversion voltages (Drain voltage for the synchronous high-side MOSFET) from 4.5 V to 24 V and output voltages from 0.76 V to 5.5 V.


HPA332 (TPS53124EVM) evaluation module is a high efficiency, dual synchronous buck converter providing 1.05 V at 4 A and 1.8 V at 4 A from 5 V to 22 V input. This user's guide describes the HPA332 performance.

2 Electrical Performance

Table 1. Electrical Performance

SPECIFICATIONS		TEST CONDITIONS	MIN	TYP	MAX	UNIT
Input voltage range (VIN)			5	12	22	V
CH1	Output voltage			1.05		V
	Operating frequency	VIN = 12 V, Iout1 = 1 A		280		kHz
	Output current			4		A
	Over current limit	VIN = 12 V		5		A
	Output ripple voltage	VIN = 12 V, Iout1 = 4 A		29		mVp-p
CH2	Output voltage			1.8		V
	Operating frequency	VIN = 12 V, Iout2 = 1 A		360		kHz
	Output current			4		A
	Over current limit	VIN = 12 V		5		A
	Output ripple voltage	VIN = 12 V, Iout2 = 4 A		33		mVp-p

3 Schematic

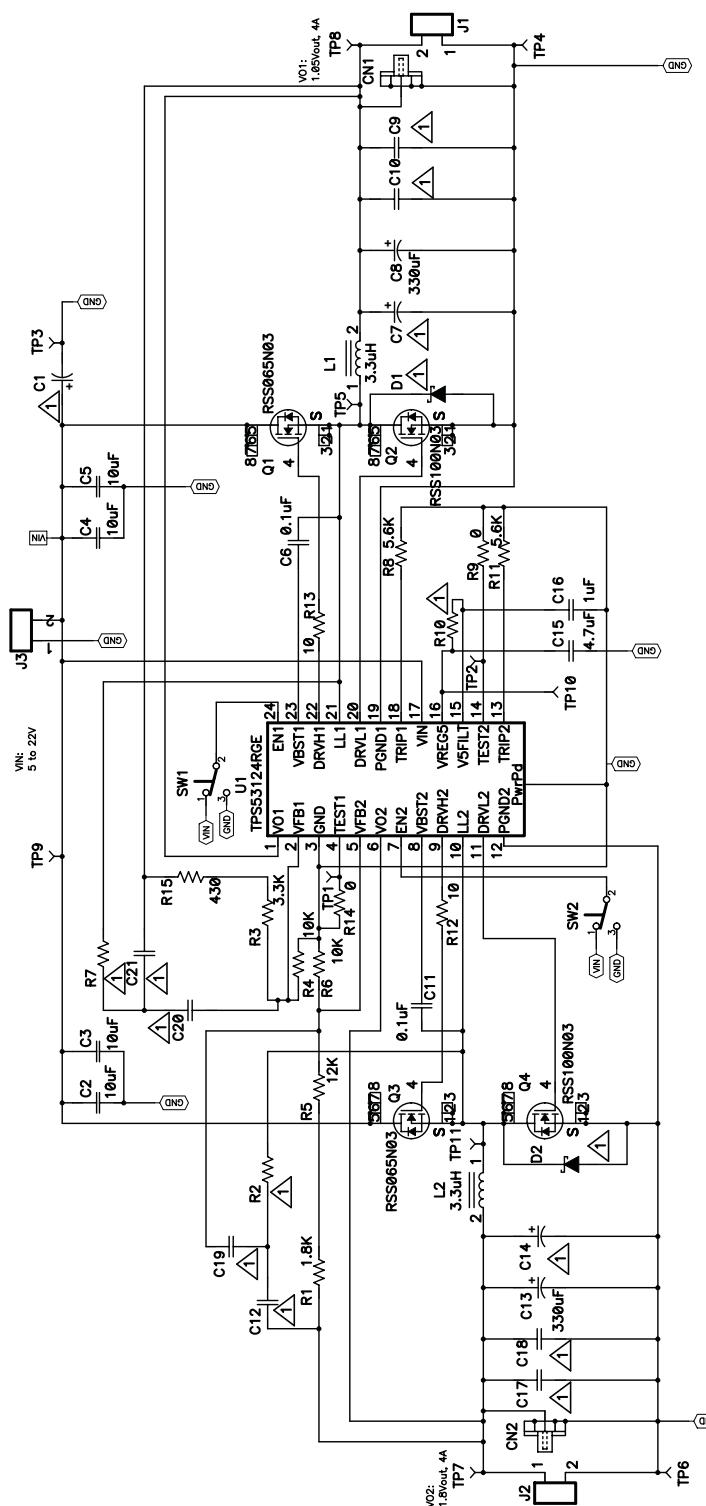

4 Test Setup and Results

4.1 Test Setup

Connect test equipment and HPA332 EVM board as shown in [Figure 2](#).

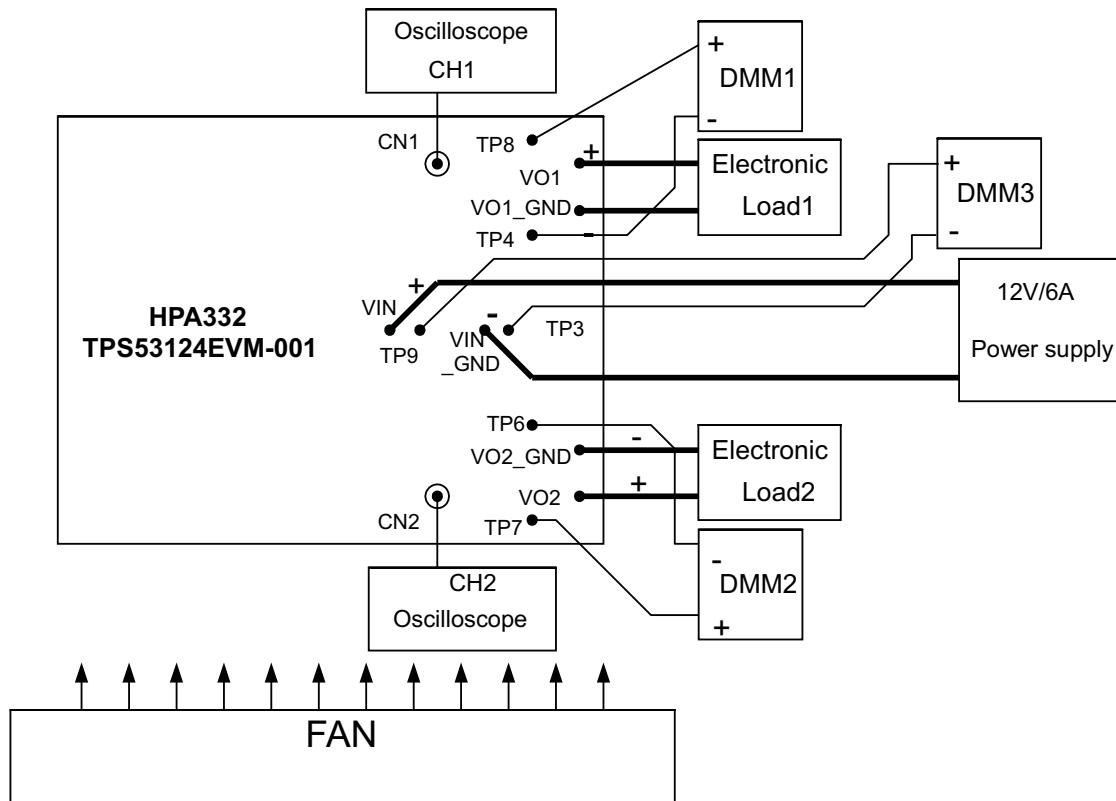


Figure 2. Equipment Setup for HPA332 EVM Board

4.2 Test Procedure

1. Make sure the switches SW1 (EN1), SW2 (EN2) are in *OFF* position.
2. Apply appropriate VIN voltage to VIN and VIN_GND terminals
3. Turn on SW1 (EN1), CH1-output will start up.
4. Turn on SW2 (EN2), CH2-output will start up.

4.3 Start Up Performance

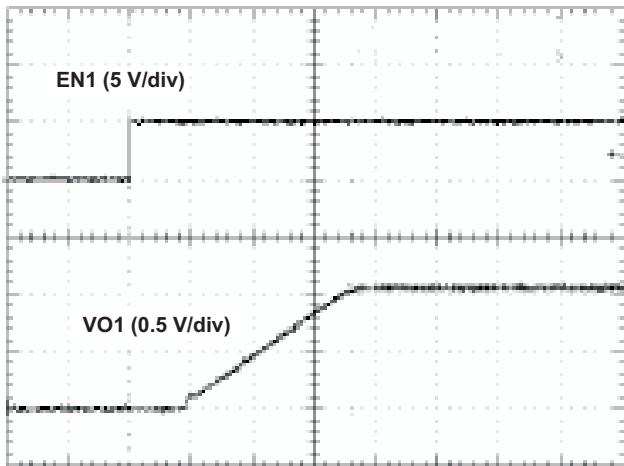


Figure 3. 1.05V Startup Waveforms

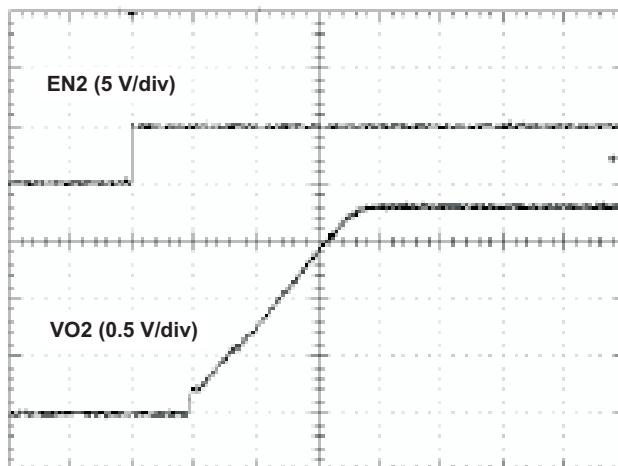


Figure 4. 1.8V Startup Waveform

4.4 Transient Response

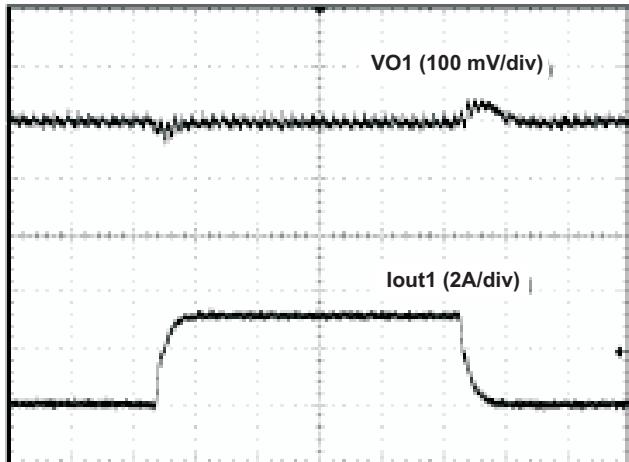


Figure 5. 1.05V Load Transient Response

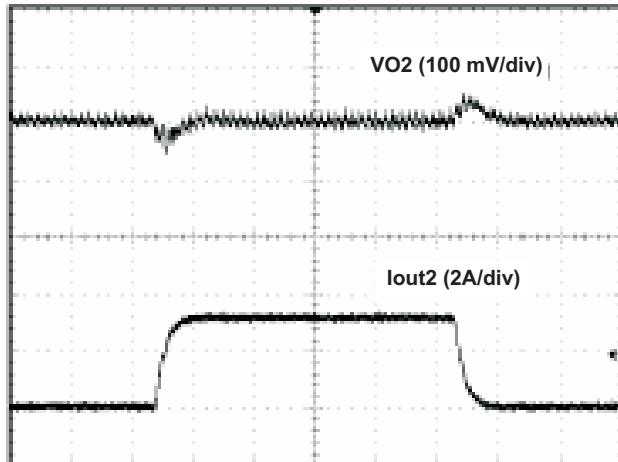


Figure 6. 1.8V Load Transient Response

5 Configuration

This EVM can be set at desired configurations. Refer to the following specific setting configuration sections.

5.1 Bootstrap Diode Selection

Bootstrap diodes are not populated on this EVM since TPS53124 has them built-in . External Schottky diodes can be added to improve efficiency.

6 EVM Assembly Drawing and PCB Layout

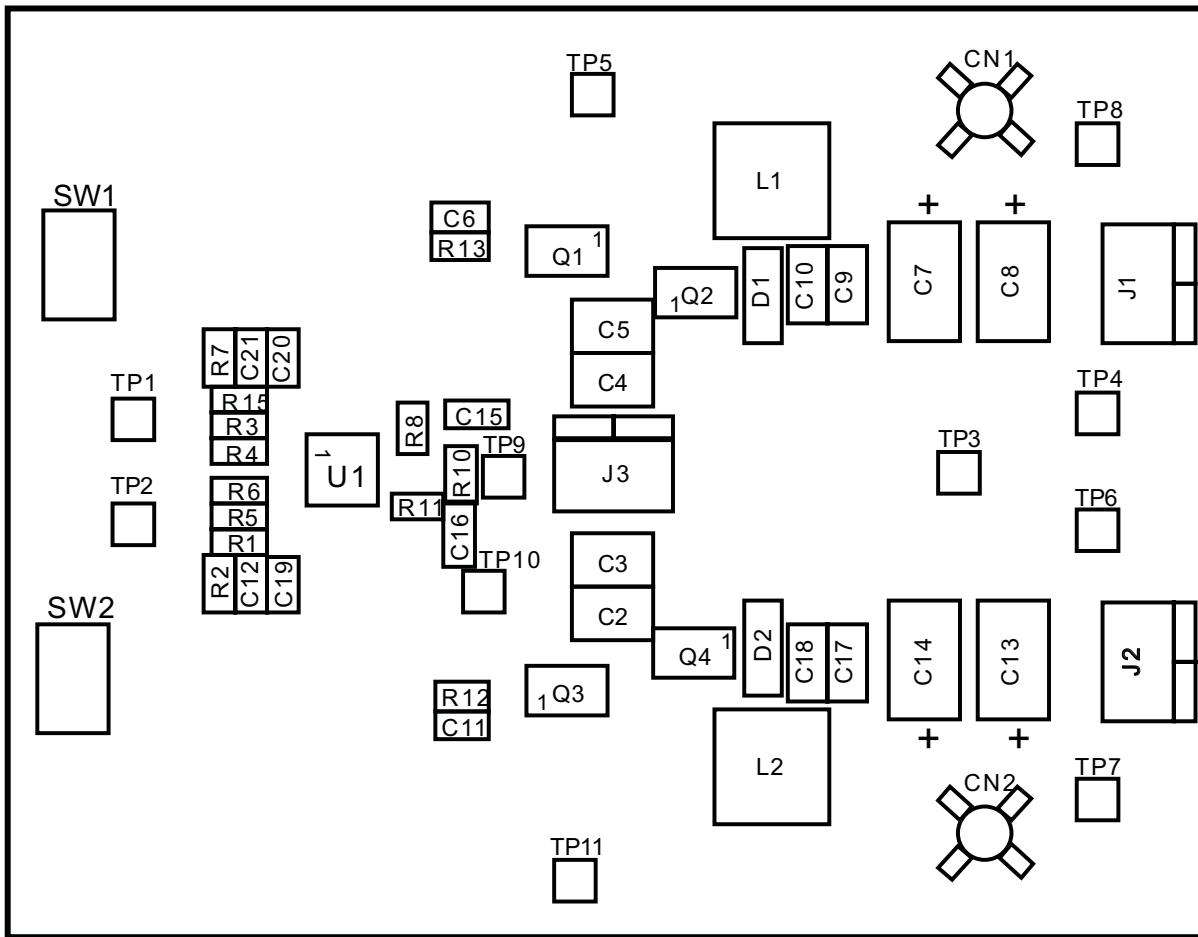


Figure 7. Top Assembly

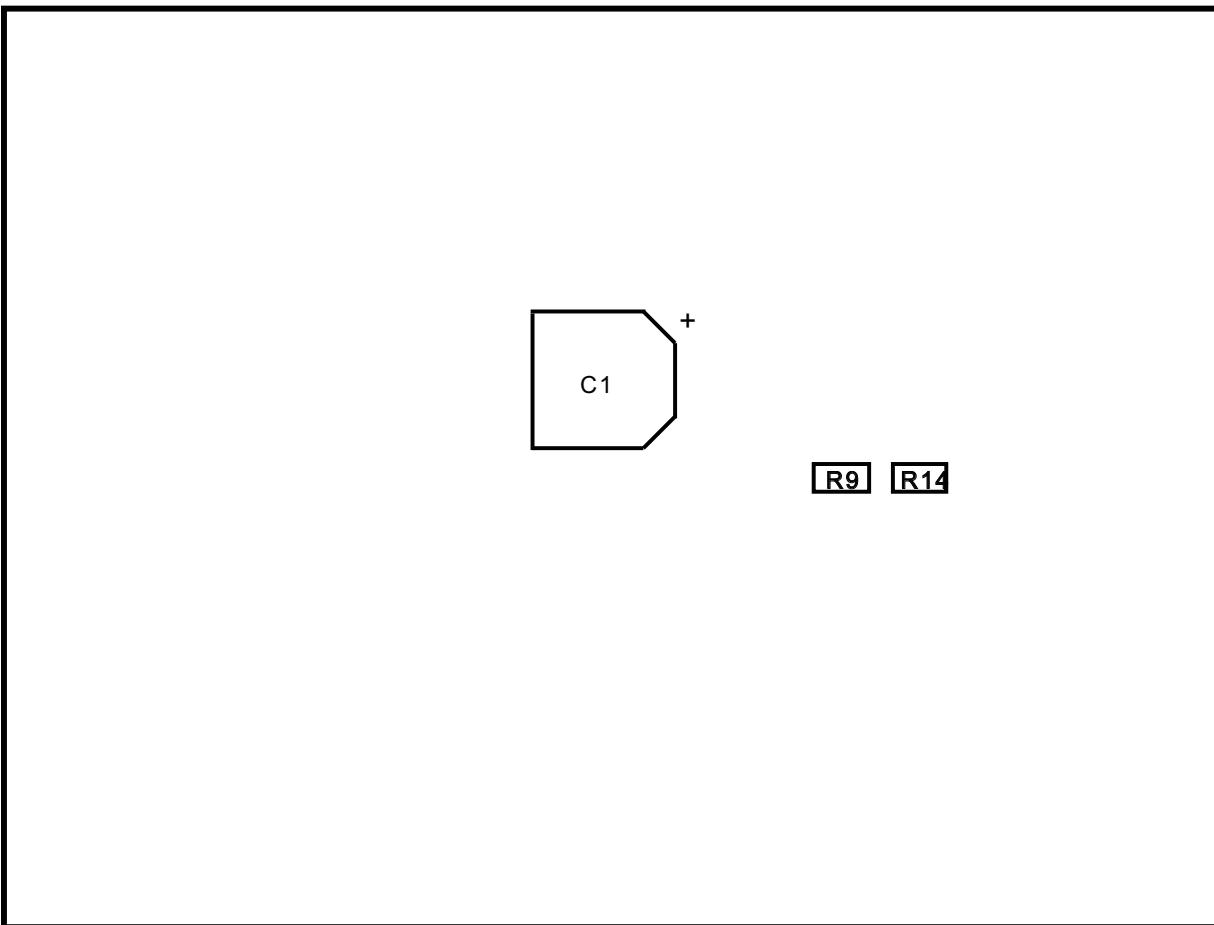


Figure 8. Bottom Assembly

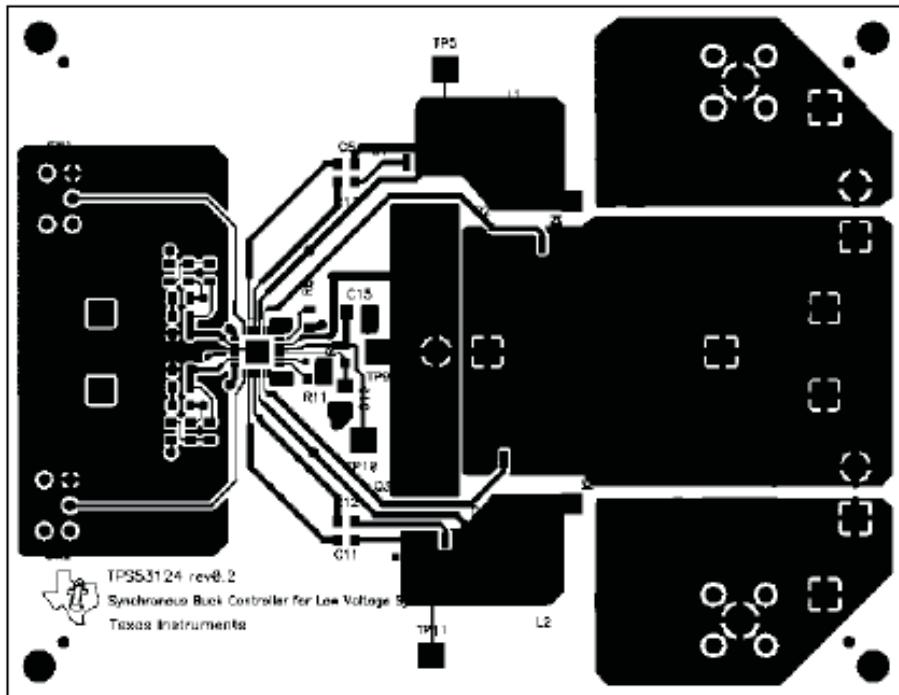


Figure 9. Top Layer

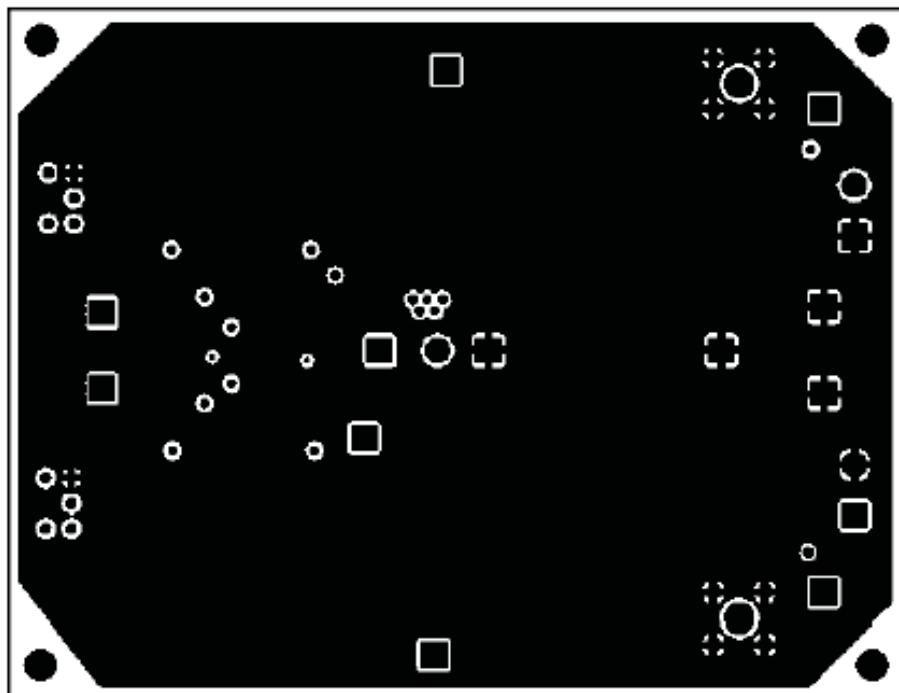


Figure 10. Inner Layer 1

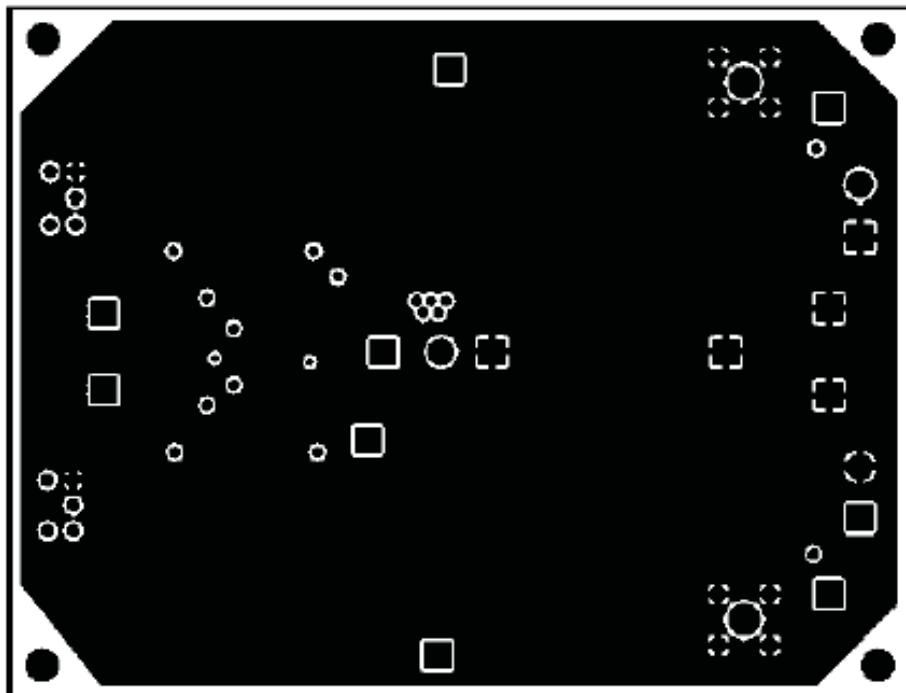


Figure 11. Inner Layer 2

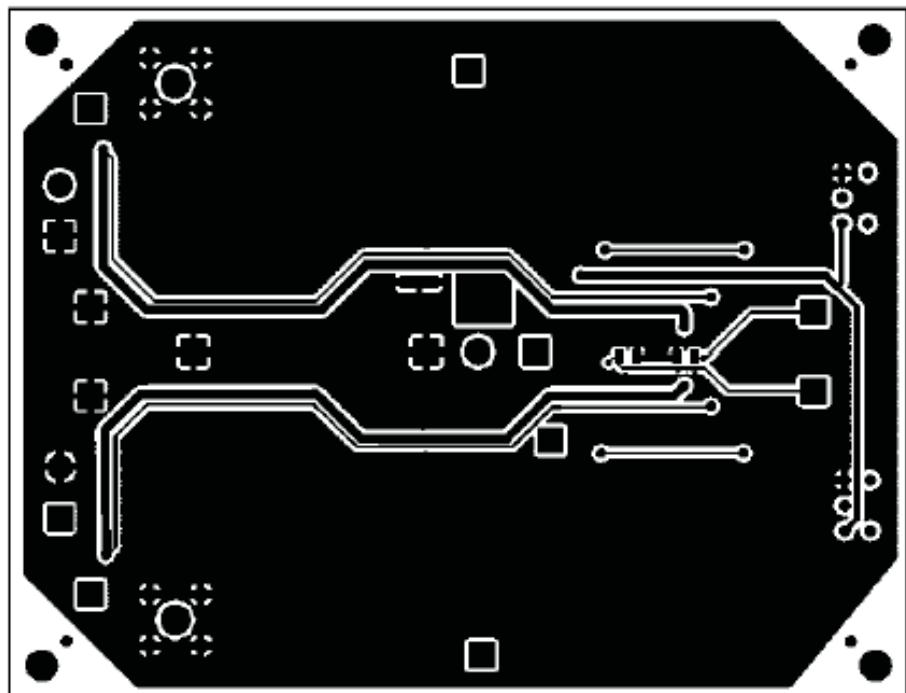


Figure 12. Bottom Layer

7 List of Materials

Table 2. List of Materials

Ref Dsg	QTY	Description	Size	MFR	Part Number
C1	0	Capacitor, Aluminum	0.26 × 0.26 inch	Any	Any
C8, C13	2	Capacitor, NPCAP, 330 µF, 4.0-V 15-mΩ , 20%	6.6 × 7.2 mm	NIPPON CHEMICON	APXE4R0ARA331M
C15	1	Capacitor, Ceramic, 4.7 µF, 10V, BJ, 20%	0805	TDK	C2012JB1A475MN
C16	1	Capacitor, Ceramic, 1 µF, 16V, BJ, 20%	0805	TDK	C2012JB1C105M75MN
C2, C3, C4, C5	4	Capacitor, Ceramic, 10 µF, 25V, BJ , 20%	1210	Taiyo Yuden	TMK325BJ106MN
C6, C11	2	Capacitor, Ceramic, 0.1 µF, 50V, BJ, 20%	0603	Std	Std
C7,C14	0	not mount	6,6 × 7,2 mm	Any	Any
C9, C10, C17,C18	0	not mount	1206	Any	Any
C12 ,C19–C21	0	not mount	0603	Any	Any
CN1, CN2	0	Adaptor, 3,5-mm probe clip (or 131-5031-00)	0.2	Tektronix	131-4244-001
D1, D2	0	Diode, Schottky, 1-A, 30-V	SMA	Any	Any
J1, J2, J3	3	Terminal Block, 2-pin, 15-A, 5,1mm	0.40 × 0.35 inch	Phoenix Contact	MKDSN1.5/2-5.08
L1, L2	2	Inductor, 3.3 µH, 6.0 A, 29.7 mΩ	6,5 × 7,1mm	TDK	SPM6530T-3R3M
Q1, Q3	2	MOSFET, N-ch, 30-V, 6.5-A, 38-mΩ	SO8	ROHM	RSS065N032
Q2, Q4	2	MOSFET, N-ch, 30-V, 10-A, 17.5-mΩ	SO8	ROHM	RSS100N03
R1	1	Resistor, Chip, 1.8 kΩ , 1/16W, 1%	0603	Std	Std
R3	1	Resistor, Chip, 3.3 kΩ , 1/16W, 1%	0603	Std	Std
R4, R6	2	Resistor, Chip, 10 kΩ , 1/16W, 1%	0603	Std	Std
R5	1	Resistor, Chip, 12 kΩ , 1/16W, 1%	0603	Std	Std
R8, R11	2	Resistor, Chip, 5.6 kΩ , 1/16W, 1%	0603	Std	Std
R9, R14	2	Resistor, Chip, 0 Ω , 1/16W, 1%	0603	Std	Std
R12, R13	2	Resistor, Chip, 10 Ω , 1/16W, 1%	0603	Std	Std
R15	1	Resistor, Chip, 430 Ω , 1/16W, 1%	0603	Std	Std
R2, R7, R10	0	not mount	0603	Any	Any
SW1, SW2	2	Switch, ON-ON Mini Toggle	0.28 × 0.18 inch	Nikkai	G12AP
TP1, TP2, TP5, TP11	4	Test Point, White, Thru Hole	0.125 × 0.125 inch	Keystone	5012
TP10	1	Test Point, Orange, Thru Hole	0.125 × 0.125 inch	Keystone	5013
TP3, TP4, TP6	3	Test Point, Black, Thru Hole	0.125 × 0.125 inch	Keystone	5011
TP7, TP8	2	Test Point, Yellow, Thru Hole	0.125 × 0.125 inch	Keystone	5014
TP9	1	Test Point, Red, Thru Hole	0.125 × 0.125 inch	Keystone	5010
U1	1	IC, Dual Synchronous Step-Down Controller for Low Voltage Power Rails,(SLUS825)	QFN24	TI	TPS53124RGE

8 Reference

1. TPS53124 Data sheet, *Dual Synchronous Step-Down Controller for Low Voltage Power Rails,(SLUS825)*

IMPORTANT NOTICE

Texas Instruments Incorporated and its subsidiaries (TI) reserve the right to make corrections, modifications, enhancements, improvements, and other changes to its products and services at any time and to discontinue any product or service without notice. Customers should obtain the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to TI's terms and conditions of sale supplied at the time of order acknowledgment.

TI warrants performance of its hardware products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are used to the extent TI deems necessary to support this warranty. Except where mandated by government requirements, testing of all parameters of each product is not necessarily performed.

TI assumes no liability for applications assistance or customer product design. Customers are responsible for their products and applications using TI components. To minimize the risks associated with customer products and applications, customers should provide adequate design and operating safeguards.

TI does not warrant or represent that any license, either express or implied, is granted under any TI patent right, copyright, mask work right, or other TI intellectual property right relating to any combination, machine, or process in which TI products or services are used. Information published by TI regarding third-party products or services does not constitute a license from TI to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from TI under the patents or other intellectual property of TI.

Reproduction of TI information in TI data books or data sheets is permissible only if reproduction is without alteration and is accompanied by all associated warranties, conditions, limitations, and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. TI is not responsible or liable for such altered documentation. Information of third parties may be subject to additional restrictions.

Resale of TI products or services with statements different from or beyond the parameters stated by TI for that product or service voids all express and any implied warranties for the associated TI product or service and is an unfair and deceptive business practice. TI is not responsible or liable for any such statements.

TI products are not authorized for use in safety-critical applications (such as life support) where a failure of the TI product would reasonably be expected to cause severe personal injury or death, unless officers of the parties have executed an agreement specifically governing such use. Buyers represent that they have all necessary expertise in the safety and regulatory ramifications of their applications, and acknowledge and agree that they are solely responsible for all legal, regulatory and safety-related requirements concerning their products and any use of TI products in such safety-critical applications, notwithstanding any applications-related information or support that may be provided by TI. Further, Buyers must fully indemnify TI and its representatives against any damages arising out of the use of TI products in such safety-critical applications.

TI products are neither designed nor intended for use in military/aerospace applications or environments unless the TI products are specifically designated by TI as military-grade or "enhanced plastic." Only products designated by TI as military-grade meet military specifications. Buyers acknowledge and agree that any such use of TI products which TI has not designated as military-grade is solely at the Buyer's risk, and that they are solely responsible for compliance with all legal and regulatory requirements in connection with such use.

TI products are neither designed nor intended for use in automotive applications or environments unless the specific TI products are designated by TI as compliant with ISO/TS 16949 requirements. Buyers acknowledge and agree that, if they use any non-designated products in automotive applications, TI will not be responsible for any failure to meet such requirements.

Following are URLs where you can obtain information on other Texas Instruments products and application solutions:

Products

Amplifiers	amplifier.ti.com
Data Converters	dataconverter.ti.com
DSP	dsp.ti.com
Clocks and Timers	www.ti.com/clocks
Interface	interface.ti.com
Logic	logic.ti.com
Power Mgmt	power.ti.com
Microcontrollers	microcontroller.ti.com
RFID	www.ti-rfid.com
RF/IF and ZigBee® Solutions	www.ti.com/lprf

Applications

Audio	www.ti.com/audio
Automotive	www.ti.com/automotive
Broadband	www.ti.com/broadband
Digital Control	www.ti.com/digitalcontrol
Medical	www.ti.com/medical
Military	www.ti.com/military
Optical Networking	www.ti.com/opticalnetwork
Security	www.ti.com/security
Telephony	www.ti.com/telephony
Video & Imaging	www.ti.com/video
Wireless	www.ti.com/wireless

Mailing Address: Texas Instruments, Post Office Box 655303, Dallas, Texas 75265
Copyright © 2008, Texas Instruments Incorporated